

# Experiment 1: Implementation and Performance Comparison of 4-bit Serial-Parallel Multiplier with Booth's Algorithm in FPGA (Xilinx's Spartan 3E Board)

Santhosh S P ee21b119 Batch 19

## 1 Serial-parallel multiplier

### 1.1 Verilog code for design of serial-parallel multiplier:

```
'timescale 1ns / 1ps
module mul_4x4(
    input [3:0] A,
    input [3:0] B,
    output reg [7:0] Product);

    always @(A or B)
    begin
        Product=8'b00000000;
        if(B[0]==1'b1)
            Product= Product+(A);

        if(B[1]==1'b1)
            Product= Product+(A<<1);

        if(B[2]==1'b1)
            Product= Product+(A<<2);

        if(B[3]==1'b1)
            Product= Product+(A<<3);

    end
endmodule
```

## 1.2 Verilog test bench code:

```
module mult_4x4_TB;
    // Inputs
    reg [3:0] A;
    reg [3:0] B;

    // Outputs
    wire [7:0] Product;
    // Instantiate the Unit Under Test (UUT)
    mul_4x4 uut (
        .A(A),
        .B(B),
        .Product(Product)
    );
    initial
        begin
            // Initialize Inputs
            A = 4'b1101;
            B = 4'b1001;
            #100;
        end
endmodule
```

### 1.3 HDL schematic of the serial-parallel multiplier:

 


Figure 1: Serial-parallel multiplier

### 1.4 Output waveforms:

 


Figure 2: A=1101, B=1001

## 2 Booth's Algorithm:

### 2.1 Verilog Design Code for Booth's algorithm:

```
'timescale 1ns / 1ps
module multiplier(prod, busy, mc, mp, clk, start);

    output [7:0] prod; // ouput 8 bits
    output busy;
    input [3:0] mc, mp; // input 4 bits
    input clk, start;
    reg [3:0] A, Q, M; // all registers are of 4 bits
    reg Q_1;
    reg [2:0] count;
    wire [3:0] sum, difference;
    always @(posedge clk)
begin
    if (start)
        begin
            A <= 4'b0000;
            M <= mc;
            Q <= mp;
            Q_1 <= 1'b0 ; // bit written to the left of lsb of number to be multiplied
            count <= 3'b0;
        end
    else
begin
        case ({Q[0], Q_1})
            2'b0_1 : {A, Q, Q_1} <= {sum[3], sum, Q};
            2'b1_0 : {A, Q, Q_1} <= {difference[3], difference, Q};
            default: {A, Q, Q_1} <= {A[3], A, Q};
        endcase
        count <= count + 1'b1;
    end
end
alu adder(sum,A,M,1'b0); // adder
alu subtracter(difference, A, ~M, 1'b1); //subtractor using 2's compliment
assign prod = {A, Q}; // make it fill up the arguments
assign busy = (count < 5);
endmodule

module alu(out, a, b, cin);
    output [3:0] out;
    input [3:0] a;
    input [3:0] b;
    input cin;
```

```

assign out = a + b + cin;
endmodule

```

## 2.2 Verilog test bench code for Booth's algorithm

```

`timescale 1ns / 1ps

module BOOTHSMULTIPLIER_TB;

// Inputs
reg [3:0] mc;
reg [3:0] mp;
reg clk;
reg start;

// Outputs
wire [7:0] prod;
wire busy;

// Instantiate the Unit Under Test (UUT)
BOOTHSMULTIPLIER uut (
    .prod(prod),
    .busy(busy),
    .mc(mc),
    .mp(mp),
    .clk(clk),
    .start(start)
);

initial begin
// Initialize Inputs
mc = 4'b1010;
mp = 4'b1110;
clk = 1;
        start = 1;
        #10 clk = ~clk;
#10 clk = ~clk;
start = 0;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
#10 clk = ~clk;
end

```

```
        $finish;
end

initial begin
    $dumpfile("BOOTHS.vcd");
    $dumpvars(0,BOOTHS_MULTIPLIER_TB);
end

endmodule
```

### 2.3 HDL schematic:

 


Figure 3: Schematic

### 2.4 Output waveforms:

 


Figure 4: mc=1010, mp=1110